



Bus

Zihao Yu


Institute of Computing Technology
Chinese Academy of Sciences

Introduction

Your CPU can communicate with some simple device models

- But in real hardware, device controllers are RTL models
- CPU should communicate with device in a hardware way

That is bus

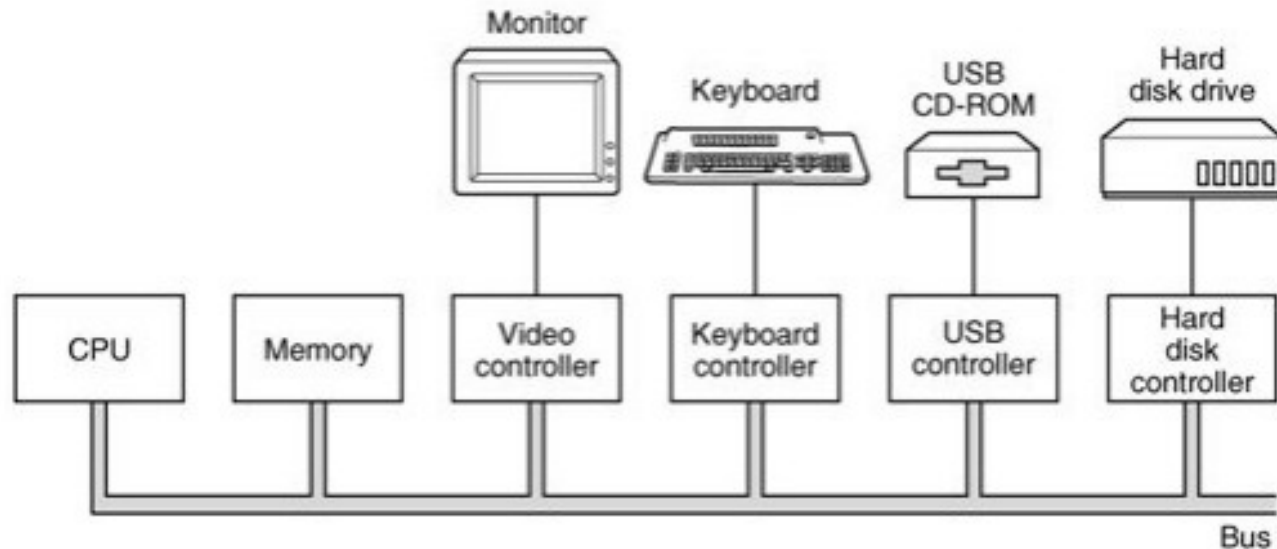

Basic Concept

Bus = Protocol

Bus is a communication protocol



- The module which starts the communication is called **master**
 - CPU
- The module which responds to the communication is called **slave**
 - MEM
- Master and slave should reach the agreement about how to communicate with each other
 - When we design master and slave, we should use circuit to implement this agreement

System Bus

Bus connecting between CPU and memory/devices

- We have already used DPI-C to emulate system bus
 - But it returns data immediately
- In the real hardware, it is not the case
 - It costs multiple cycles to get the data

This requires CPU to implement the following:

1. identify when the data returns from memory
2. wait until the data returns
 - after that, CPU can continue to execute the instruction
3. tell memory when CPU should fetch an instruction
 - When CPU is waiting, it should not issue any new fetch requests

Simple Bus (2)

Real chips usually adopt industry protocol like AXI

- It contains about 30 signals, which is complicated

For simplicity, we define a simple bus protocol called SimpleBus

- We will provide a bridge later to convert SimpleBus into AXI
 - Then integrate your CPU into SoC to communicate with other devices

Let us start with a simple case

Measure the Performance of CPU

Before starting to discuss bus, we first try to measure the performance of your CPU

TASK 1 - Computer IPC (Instruction Per Cycle) for your CPU

- Computer how many instructions and cycles your CPU costs to execute a program
- Then compute `inst / cycle`
 - It should be around `1`

You will measure IPC again after you implement bus

Fetch Instructions with Delay

The Protocol

Assume that the delay of accessing memory is 1 cycle

- CPU sends `raddr` to memory, and gets `rdata` in the next cycle

```
+-----+ raddr[log2(N)-1:0] ---> +-----+  
| CPU | <---          rdata[31:0] | MEM |  
+-----+                       +-----+
```

Both instruction fetch and load/store will access memory

- To distinguish between them, we refer the corresponding units as IFU and LSU
 - IFU = Instruction Fetch Unit, LSU = Load/Store Unit

For IFU, SimpleBus involves the following signals:

```
output [31:0] ifu_raddr,  
input  [31:0] ifu_rdata,
```

Timing Diagram

```
--\ /-----\ /-----\ /-----\ /-----\ /--
ifu_raddr      X 0x80000000 X      (1)      X 0x80000004 X      X
--/ \-----/ \-----/ \-----/ \-----/ \--
ifu_rdata      X      X 0x00000413 X      (2)      X 0x80051137 X
--/ \-----/ \-----/ \-----/ \-----/ \--
```

Implement Waiting

	Stage 1				Stage 2				Stage 1				Stage 2			
	--\	/	-----	\	/	-----	\	/	-----	\	/	-----	\	/	-----	\
ifu_raddr	X		0x80000000	X		(1)		X		0x80000004	X					X
	--/	\	-----	/	\	-----	/	\	-----	/	\	-----	/	\	-----	/
	--\	/	-----	\	/	-----	\	/	-----	\	/	-----	\	/	-----	\
ifu_rdata	X			X		0x00000413	X			(2)		X		0x80051137	X	
	--/	\	-----	/	\	-----	/	\	-----	/	\	-----	/	\	-----	/

We should let IFU know which stage it is at

- IFU should do different things in different stages

This can be implemented by **state machine** in digital circuit

Define two states - **idle** and **wait**

- At **idle** state: set **ifu_raddr** to the current PC, and switch to **wait** state
- At **wait** state: get **ifu_rdata** as an instruction to execute, and switch to **idle** state

Implement Waiting(2)

	idle	wait	idle	wait
ifu_raddr	--\ /-----\ /-----\ /-----\ /-----\ /--			
	X 0x80000000 X	(1)	X 0x80000004 X	X
	--/ \-----/ \-----/ \-----/ \-----/ \--			
ifu_rdata	--\ /-----\ /-----\ /-----\ /-----\ /--			
	X	X 0x00000413 X	(2)	X 0x80051137 X
	--/ \-----/ \-----/ \-----/ \-----/ \--			

At `idle` stage, `ifu_rdata` is not a valid instruction

- There is no instruction for CPU to execute
- But how to make CPU not execute any instruction?
- The behavior of executing an instruction: change the state of CPU
 - change GPR and PC
- If we keep the state of PC unchanged, it is equivalent to not executing any instruction
 - Solution - disable the write enable signals for GPR and PC

Let IFU support SimpleBus

TASK 2 - let IFU support SimpleBus

- Let memory delay 1 cycle to return the result for instruction fetch

```
always @(posedge clock) begin
    ifu_rdata <= mem_read(ifu_raddr);
end
```

- Implement the SimpleBus Protocol in IFU
- Leave LSU unchanged now
 - We will change it in the following tasks
- Try to run some programs
 - The results should be the same as before
 - Since bus protocol should be transparent to the program
 - But you can check the waveform to confirm the timing of the communication
- Compute IPC

Access Data with Delay

Support Write Request

We should add new signals to the protocol to carry a write request

- `waddr` for write address
- `wdata` for write data
- `wen` for write enable
- `wmask` for write mask

```
+-----+ addr[log2(N)-1:0] ---> +-----+
|       | wen                ---> |       |
| CPU   | wdata[31:0]         ---> | MEM   |
|       | wmask[3:0]          ---> |       |
|       | <---              rdata[31:0] |       |
+-----+                        +-----+
```

We can combine `raddr` and `waddr` to get `addr`

- Since LSU will not issue read request and write request at the same time


SimpleBus for LSU

For LSU, SimpleBus involves the following signals:


```
output [31:0] lsu_addr,  
output      lsu_wen,  
output [31:0] lsu_wdata,  
output [ 3:0] lsu_wmask,  
input  [31:0] lsu_rdata,
```

Timing Diagram for Read

wdata and wmask can be any value

 

Timing Diagram for Write

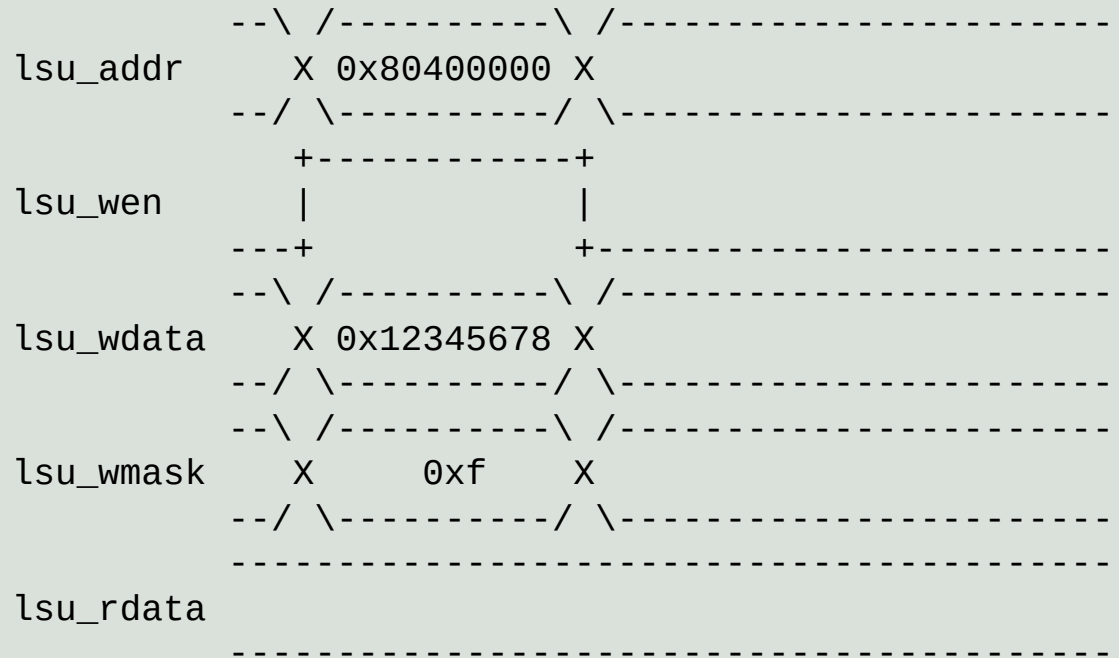

Let LSU support SimpleBus

TASK 3 - let LSU support SimpleBus

- Let memory delay 1 cycle to return the result for load

```
always @(posedge clock) begin
    lsu_rdata <= (!lsu_wen) ? mem_read(lsu_addr) : 32'b0;
    if (lsu_wen) begin
        mem_write(lsu_addr, lsu_wdata, lsu_wmask);
    end
end
```

- Implement the SimpleBus protocol in LSU
 - For load, IFU should fetch next instruction after the load data is back
- Leave the device models unchanged now
 - We will change them to real device controllers in the SoC
- Try to run some programs
- Compute IPC

Support Delay > 1 cycle

Larger and Slower Memory

For more types of memory, access delay will be larger

- You may not know the actual delay in advanced
 - It depends on the internal state of the memory
- Memory should tell CPU when the access finishes
 - add a new signal `respValid`
- CPU should also tell Memory when there is a valid request
 - add a new signal `reqValid`

SimpleBus Supporting Delay > 1 cycle


```
+-----+ reqValid          ---> +-----+
|       | addr[log2(N)-1:0] ---> |       |
|       | wen              ---> |       |
| CPU   | wdata[31:0]      ---> | MEM   |
|       | wmask[3:0]       ---> |       |
|       | <---            respValid |       |
|       | <---            rdata[31:0] |       |
+-----+                    +-----+
```

Take LSU as an example, SimpleBus now involves the following signals:

```
output      lsu_reqValid,
output [31:0] lsu_addr,
output      lsu_wen,
output [31:0] lsu_wdata,
output [ 3:0] lsu_wmask,
input       lsu_respValid,
input [31:0] lsu_rdata,
```


Timing Diagram for Read

wdata and wmask can be any value

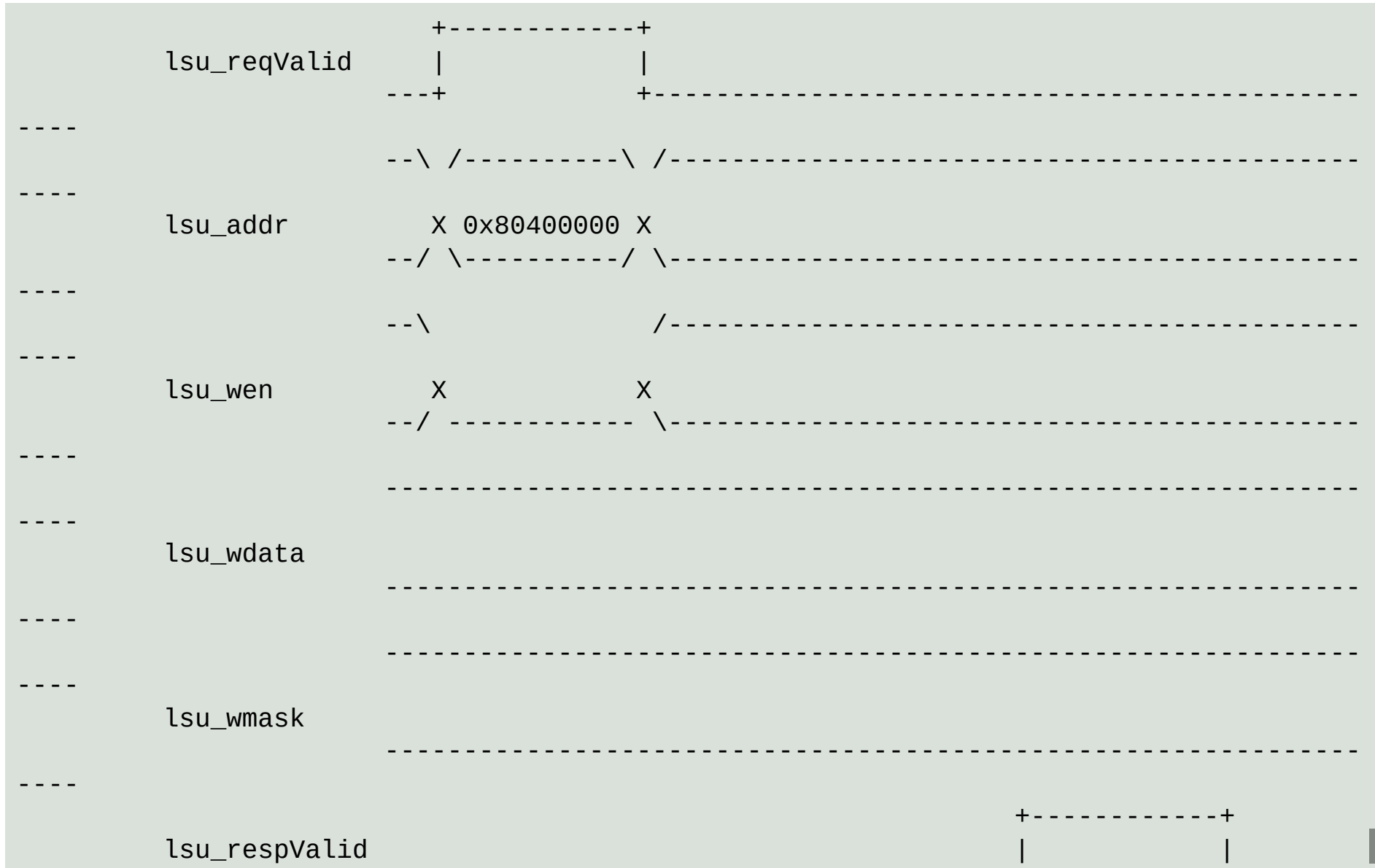

Timing Diagram for Write

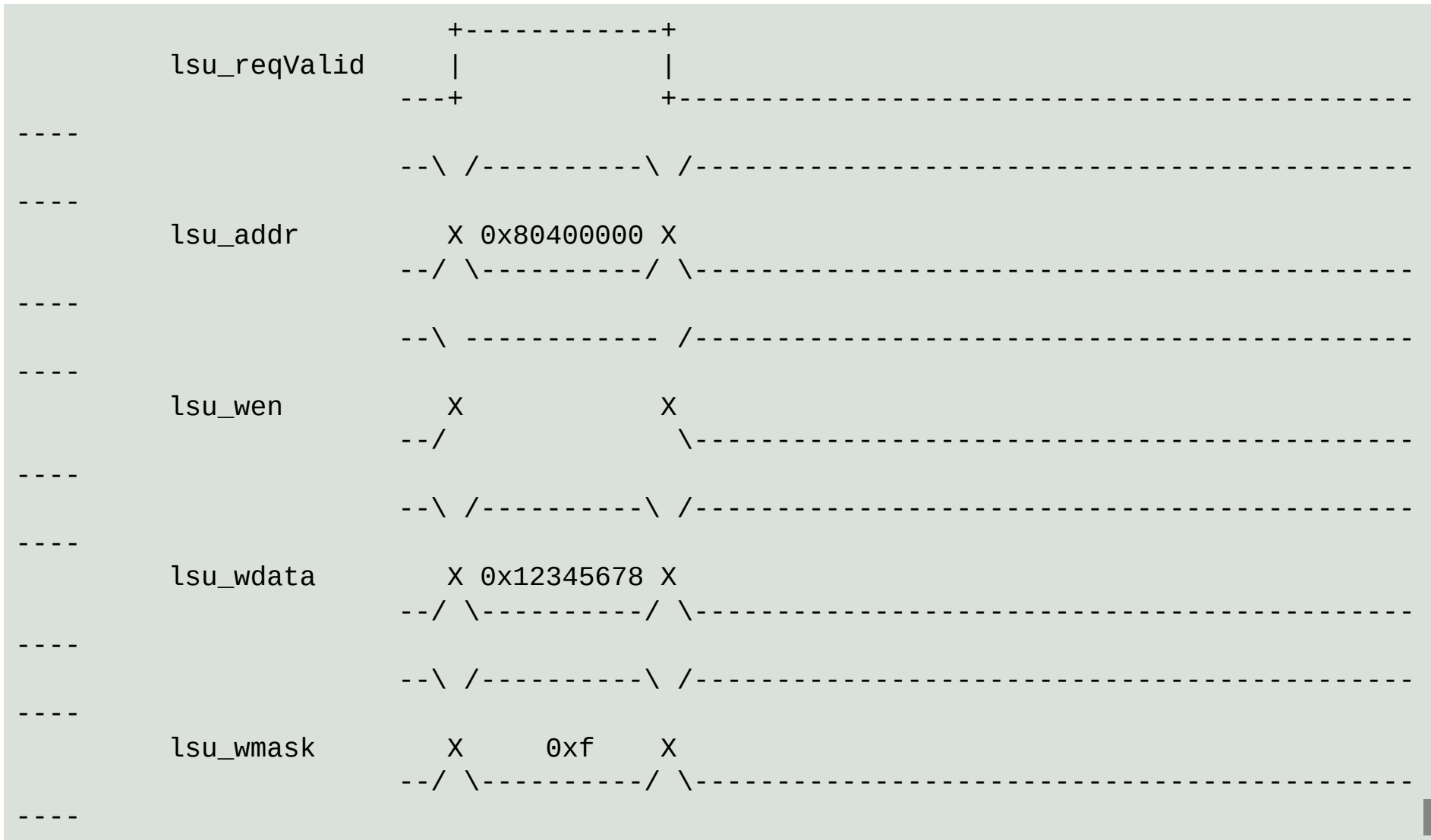Although `rdata` is irrelevant for write, SimpleBus still sets `respValid` to high to indicate when a write request finished



Extend the State Machine

To support `reqValid` and `respValid`, we should modify the state machine (take read as example):

- At `idle` state
 - If CPU wants to access memory, then set `reqValid` and `addr`, and switch to `wait` state
 - If CPU does not want to access memory, then stay at `idle` state
- At `wait` state
 - If `respValid` is high, then get the data from `rdata`, and switch to `idle` state
 - If `respValid` is low, then stay at `wait` state

For write, CPU should also wait for `respValid`

Support SimpleBus with Valid Signals

TASK 4 - support SimpleBus with valid signals

- Modify the slave for LSU as following

```
always @(posedge clock) begin
    lsu_rdata <= (lsu_reqValid && !lsu_wen) ? mem_read(lsu_addr) : 32'b0;
    if (lsu_reqValid && lsu_wen) begin
        mem_write(lsu_addr, lsu_wdata, lsu_wmask);
    end
    lsu_respValid <= lsu_reqValid;
end
```

- Modify the slave for IFU in a similar way, but without write
- Implement the new SimpleBus protocol in IFU and LSU
- Try to run some programs
- Compute IPC

More Testing

TASK 5 - do more testing to your code

1. Modify the access delay to 5/10/20 cycles
2. Perform some random testing
 - Implement a LFSR (Linear-feedback shift register)
 - Ask Google or AI
 - Take the random values generated by LFSR to determine the access delay
 - When `respValid` is low, fill `rdata` with random value
3. Add LFSR in IFU and LSU to add random delay to the `reqValue` signals

END

